

EE203 - Electrical Circuits Laboratory


Experiment - 8 Laboratory Report
RLC Circuits

Name: Korkut Emre Arslantürk
Submission Date: 19/01/2021

Number: 250206039

Preliminary Work

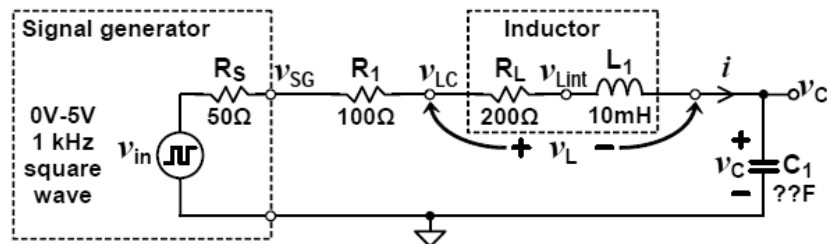1. In the following circuit internal resistance of the inductor is shown as $R_L = 200 \Omega$. Output resistance $R_S = 50 \Omega$ of the signal generator and R_L should be included in the calculations when they are comparable to the external resistance R_1 .



1.a) Calculate the capacitance C_1 that gives the resonance frequency $f_o = 50 \text{ kHz}$.

$$a) f_o = \frac{1}{2\pi\sqrt{LC}} = 50 \text{ kHz}, \text{ also we know } L = 10 \text{ mH}$$

So we can find C easily.

$$C \times 10 \times 10^{-3} \text{ H} = \frac{1}{(100\pi \times 10^2)^2} \Rightarrow C = 1.01 \text{ nF}$$

1.b) Calculate the damped oscillation frequency $f_d = \omega_d/2\pi$, and the decay time constant τ for $R_1 = 0 \Omega$, 100Ω , and $1 \text{ k}\Omega$.

b) For $R_1 = 0 \Omega$,

$$\tau = \frac{2L}{R} = 80 \times 10^{-6} \text{ s}$$

$$\Rightarrow f_d = \frac{\sqrt{\left(\frac{1}{(0.01)(1.01 \times 10^{-9})}\right)^2 - \left(\frac{250}{4(0.01)^2}\right)^2}}{2\pi} = 50.3 \text{ kHz}$$

For $R_1 = 100 \Omega$,

$$\tau = \frac{2L}{R} = 57.1 \times 10^{-6} \text{ s}$$


$$f_d = \frac{\sqrt{1.013 \times 10^{11} - \left(\frac{250}{4(0.01)^2}\right)^2}}{2\pi} = 50.26 \text{ kHz}$$

For $R_1 = 1 \text{ k}\Omega$

$$\tau = \frac{2L}{R} = 16 \times 10^{-6} \text{ s}$$

$$f_d = \frac{\sqrt{1.13 \times 10^{11} - \left(\frac{1250}{4(0.01)^2}\right)^2}}{2\pi} = 49.5 \text{ kHz}$$

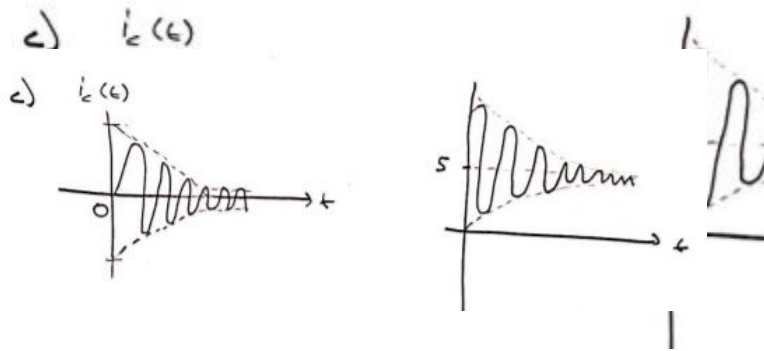1.c) Draw $i(t)$ and $v_C(t)$ as a function of time after v_{in} switches from 5 V to 0 V, for



1.d) Calculate the R_1 value that gives the critically damped response.

d) For critically damped response,

$$\alpha = \omega_0 \rightarrow R = 2 \sqrt{\frac{L}{C}} = 2 \sqrt{\frac{0.01}{1.013 \times 10^{-9}}} = 6.2 \text{ k}\Omega$$

2. Consider the RLC circuit given above when $v_{in} = 2.5 \text{ V} \sin(\omega_d t)$.

Calculate steady state $i(t)$, $v_C(t)$, and $v_{L_C}(t)$ when $R_1 = 0 \Omega$, 100Ω , and $1 \text{ k}\Omega$.

For $R_1 = 0 \Omega$

$$Q = \frac{\sqrt{L/C}}{R} = \frac{\sqrt{1.032 \times 10^{-9} / (10 \times 10^{-3})}}{250} = \frac{0.312 \times 10^3}{250}$$

So, $v_{L_C}(t) = 0$ for average.

$$i_C(t) = \frac{2.5}{250} = 10 \text{ mA}, \quad v_C(t) = Q \times 2.5 \sin(\omega_d t) \times \angle -90^\circ$$

$$= \frac{8105}{250} \cos(\omega_d t) = 32.42 \cos(\omega_d t) \text{ V}$$

$$v_{L_C}(t) = 1.99 \cos(\omega_d t) \text{ V}$$

For $R_1 = 100 \Omega$

$$Q = \frac{\sqrt{L/C}}{R} = \frac{1}{350} \times \sqrt{\frac{1.032 \times 10^{-9}}{10 \times 10^{-3}}} = 0.917$$

$$i(t) = \frac{2.5}{350} \sin(\omega_d t) = 7.15 \sin(\omega_d t) \text{ mA}$$

$$v_C(t) = Q \times 2.5 \sin(\omega_d t) = 22.945 \cos(\omega_d t), \quad v_{L_C}(t) = 1.4 \cos(\omega_d t) \text{ V}$$


For $R_1 = 1 \text{ k}\Omega$

$$Q = \frac{\sqrt{L/C}}{R} = \frac{1}{1250} \times \sqrt{\frac{1.032 \times 10^{-9}}{10 \times 10^{-3}}} = 2.6, \text{ Thus } v_C(t) = 6.42 \cos(\omega_d t)$$


$$i(t) = \frac{2.5}{1250} = 2 \sin(\omega_d t) \text{ mA}, \quad v_{L_C}(t) = 0.4 \cos(\omega_d t) \text{ V}$$

Procedure

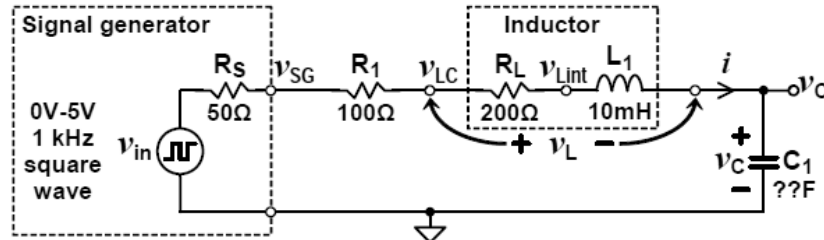1. Set up the circuit given below using the capacitance C_1 calculated in the preliminary work and set the v_{in} signal source to obtain **1 kHz** square wave that switches between **0 V** and **5 V** with the timing parameters, $T_{rise} = 1n$, $T_{fall} = 1n$, $T_{on} = 500u$, and $T_{period} = 1m$. Set simulation time to **1 ms**.



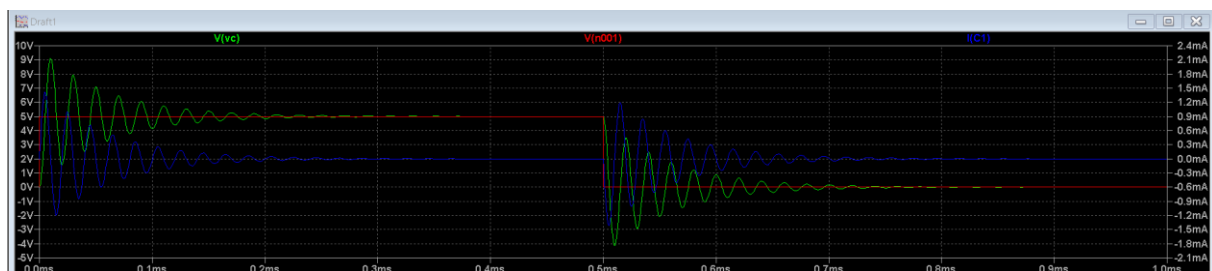1.1 Display v_{in} , $v_C(t)$ and $i(t)$ waveforms and plot $v_C(t)$ and $i(t)$ waveforms.



1.2 Measure the v_C oscillation frequency $f_d = 1/T_d$, and the decay time constant τ for the R_1 values given in the following table.


R_1	f_d (Hz)	τ (μs)
0 Ω	50.00KHz	75.28 μs
100 Ω	50.05KHz	55.10 μs
1 kΩ	49.60KHz	15.79 μs

1.3 Observe $i(t)$ and $v_C(t)$ for several R_1 values around the resistance calculated for critically damped response in the preliminary work step 1.d.

Determine the R_1 resistance that gives the critically damped response by changing R_1 in **0.1 k Ω** steps. Monitor v_C as you increase the R_1 resistance until the overshoot at the rising v_C edge disappears. Zoom into the v_C waveform to see the circuit response clearly.

$$R_1 = 5.9k \Omega$$


$$R_1 + 250 \Omega = 6150 \Omega$$

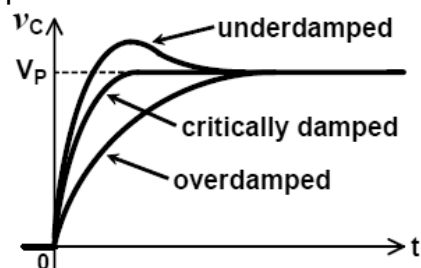

2.b) Simulate the circuit in LTspice and verify your calculations.


- Observe $i(t)$, $v_C(t)$, and $v_{LC}(t)$ for $R_1 = 0 \Omega$, 100Ω , and $1 k\Omega$, and compare the steady state peak values with your calculations.

For $R_1=0 \Omega$:

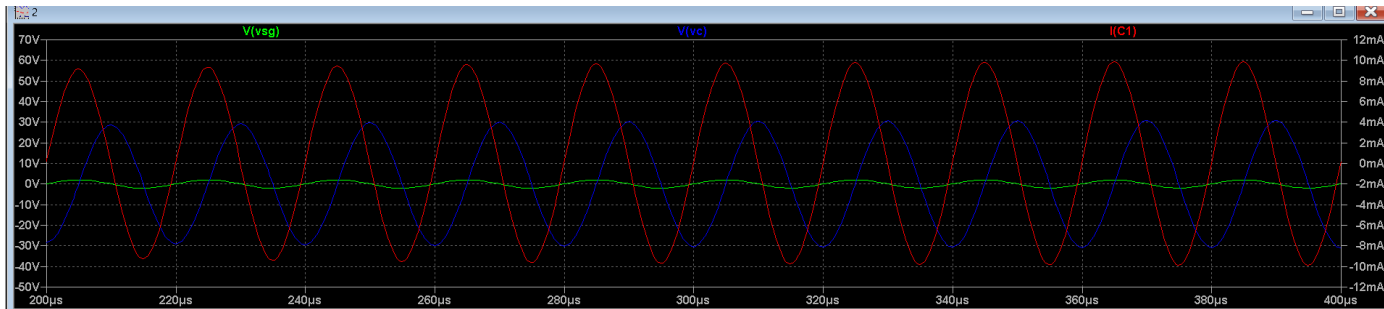


	Measured values in simulation	Calculated values in preliminary work	%error
$v_{LC} (V)$	1.98V	1.99V	0.5
$i (mA)$	9.94mA	10 mA	0.6
$v_C (V)$	31.08V	32.42 V	4.1

For $R_1=100 \Omega$:

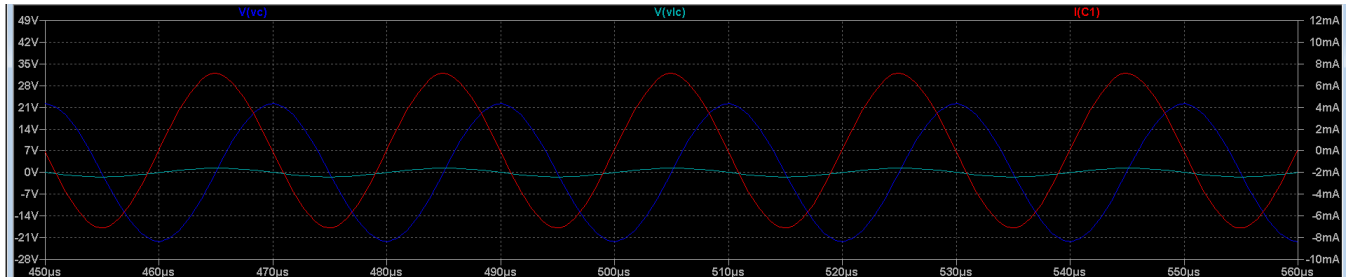

	Measured values in simulation	Calculated values in preliminary work	%error
$v_{LC}(V)$	1.42V	1.4 V	1.4
$i (mA)$	7.11mA	7.15 mA	0.56
$v_C (V_p)$	22.26V	22.94 V	3.05


For $R_1=1k \Omega$:

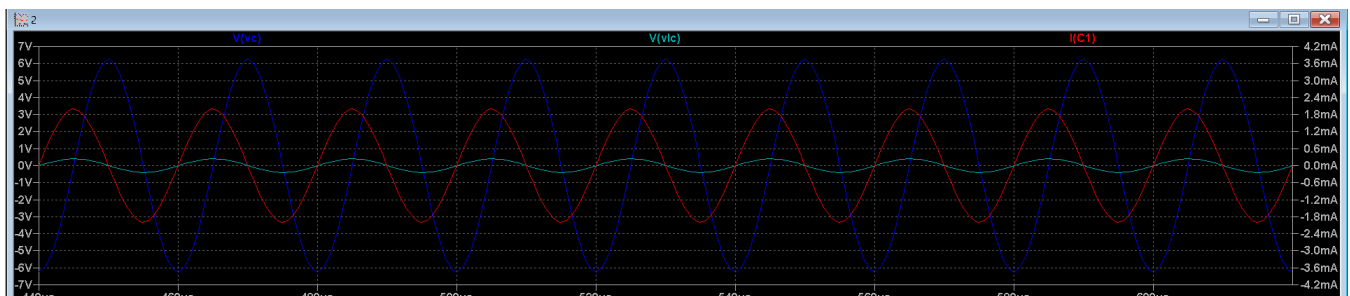


	Measured values in simulation	Calculated values in preliminary work	%error
$v_{Lc}(V)$	0.395V	0.4 V	1.25
i (mA)	1.99mA	2 mA	0.5
$v_c(V)$	6.225V	6.42 V	3.03

Our percentage of error is fewer than %5 for every values. This little bit error can be because of decimal rounding or cursor error while measuring.

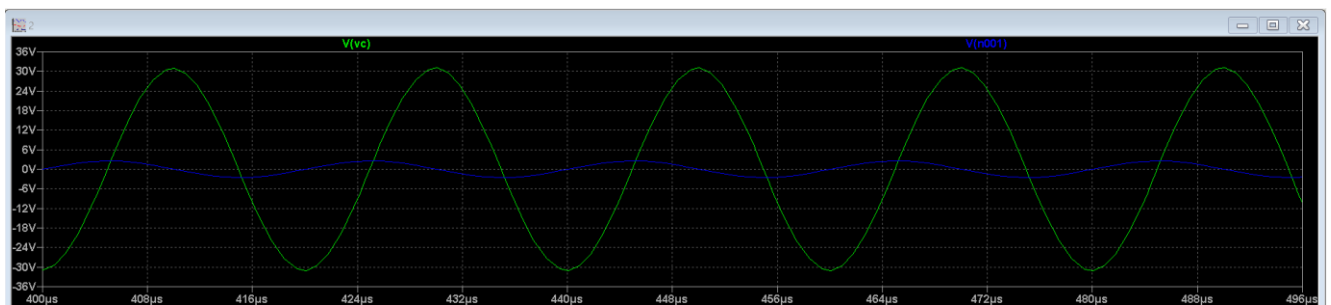2. Setup the circuit given for step-1 with $R_1 = 0 \Omega$, and set the v_{in} signal source to obtain **5 Vp-p** sine wave at the resonance frequency found in step-1.



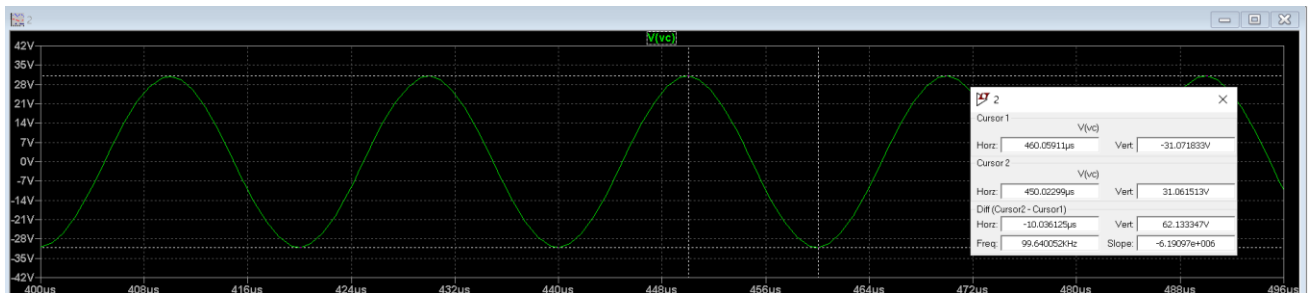2.1 Observe v_c waveform and change the signal generator frequency in **100 Hz** steps to obtain the maximum peak-to-peak voltage at v_c .




Maximum $v_c = 62.13V$

at frequency = 50kHz

2.2 Observe $v_{Lint}(t)$ (voltage between R_L and L in the inductor), and find the v_{in} frequency that makes steady state amplitude of $v_{Lint} = 0$. Start with the frequency found in 2.1 and change v_{in} frequency in **50 Hz** steps.

Frequency where $v_{Lint} = 0 = 50050Hz$

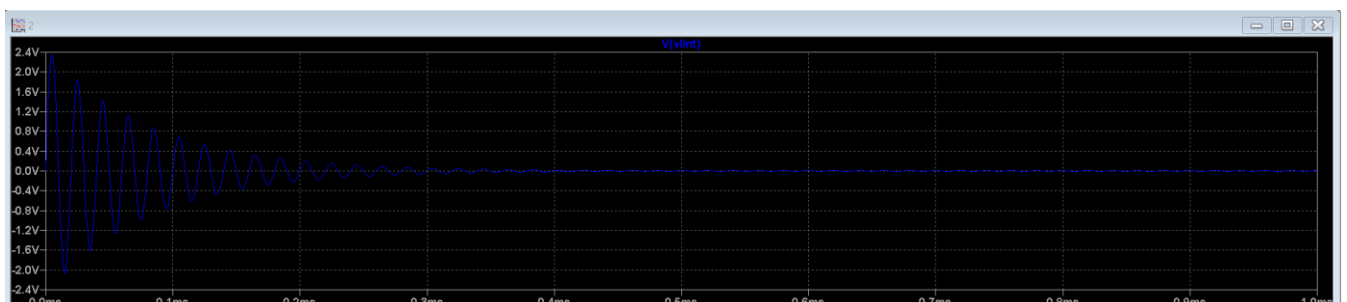

2.3 Measure the following peak-to-peak voltage and current values while the signal source voltage and frequency settings are kept the same.

R_1	V_{SG} (Vp-p)	V_{LC} (Vp-p)	i (mA p-p)	V_C (Vp-p)
0 Ω	3.98V	3.98V	19.88mA	62.17V
100 Ω	4.27V	2.84V	14.22mA	44.51V
1 kΩ	4.78V	0.79V	3.98mA	12.45V

Questions

Q1. Compare the oscillation frequency f_d , and the decay time constant τ measured in procedure step-1.2 with values calculated in the preliminary work.

		Measured values in simulation step 1.2	Calculated values in preliminary work	%error
oscillation frequency f_d	0 Ω	50.00KHz	50.3KHz	0.6
	100 Ω	50.05KHz	50.26KHz	0.4
	1 kΩ	49.60KHz	49.5KHz	1.01
decay time constant τ	0 Ω	75.28 μ s	80 μ s	4.9
	100 Ω	55.10 μ s	57.1 μ s	3.5
	1 kΩ	15.79 μ s	16 μ s	1.3

Our percentage of error is fewer than %5 for every values. This little bit error can be because of decimal rounding or cursor error while measuring.

Q2. Compare the resistance found in procedure step-1.3 with the resistance calculated for critically damped response in the preliminary work.

	Measured values in simulation step 1.2	Calculated values in preliminary work	%error
resistance for critically damped response	6150 Ω	6200 Ω	0.8

Our percentage of error is fewer than %5 for every values. This little bit error can be because of decimal rounding or cursor error while measuring.

Q3. Compare the peak-to-peak voltage and current values measured in procedure step-2 with the results found in the preliminary work (remember the difference between **peak-to-peak** and **peak** values).

For $R_1=0\ \Omega$:

	Measured values in simulation	Calculated values in preliminary work	%error
$v_{Lc}\ (V)$	3.98V	3.98V	0.5
$i\ (mA)$	19.88mA	20 mA	0.6
$v_C\ (V)$	62.17V	64.84 V	4.1

For $R_1=100\ \Omega$:

	Measured values in simulation	Calculated values in preliminary work	%error
$v_{Lc}(V)$	2.84V	2.8 V	1.4
$i\ (mA)$	14.22mA	14.3 mA	0.56
$v_C\ (Vp)$	44.51V	44.88 V	3.05

For $R_1=1k\ \Omega$:

	Measured values in simulation	Calculated values in preliminary work	%error
$v_{Lc}(V)$	0.79V	0.8 V	1.25
$i\ (mA)$	3.98mA	4 mA	0.5
$v_C(V)$	12.45V	12.84 V	3.03

Our percentage of error is fewer than %5 for every values. This little bit error can be because of decimal rounding or cursor error while measuring.

Q4. How is it possible to obtain a capacitor voltage much higher than the signal generator output in procedure step-2?

We know, impedance of capacitor is inversely proportional with frequency, also we know, impedance of inductor is directly proportional with frequency. The series circuit's inductive as: $X_L > X_C$, at higher frequency values. According to that we see lagging power factor and because of that we get much higher output voltage than input voltage.

Q5. The same resonance frequency can be obtained when L_1 and C_1 are replaced by $10 L_1$ and $0.1 C_1$, or by $0.1 L_1$ and $10 C_1$ in procedure step-2. In which of these cases a higher $v_c(t)$ amplitude is obtained? Why?

According to second situation($0.1 L_1$ and $10 C_1$), the series circuit's inductive like: $X_L > X_C$, and because of this situation we get lagging power factor at higher frequency values. If the capacitance value is increased and the inductance value is reduced, the efficiency factor will be reduced. Therefore, we get the lower amplitude of V_c . In order to achieve a higher V_c amplitude, we can replaced L_1 and C_1 with $10L_1$ and $0.1C_1$.

Conclusion

In this experiment, firstly we set given circuit in figure 1 and we set the V_{in} signal source to obtain 1kHz square wave that switches between 0V and 5V. Then we displayed V_{in} , $V_c(t)$ and $i(t)$ waveforms. Then we measured oscillation frequency and decay time constant values for different R_1 values(0Ω, 100Ω, 1kΩ). Then we determined the R_1 resistance value that gives the critically damped response. We increased R_1 resistance until the overshoot at the rising V_c edge disappears to get that. Then we compared our simulation results and calculated values in preliminary work according to peak values of $I(t)$, $V_c(t)$ and $V_{LC}(t)$. Then we set up the circuit given for step 1 with $R_1=0 \Omega$ and we set the V_{in} signal source to obtain $5V_{p-p}$ sine wave at the resonance frequency. After that, we observed maximum V_c peak to peak value and its frequency. After that we found frequency value of $V_{L_{int}}=0$. After that, we measured peak to peak values of V_{SG} , V_{LC} , i , V_c for different R_1 values(0Ω, 100Ω, 1kΩ) and we compared them with preliminary work results.

To sum up in this experiment, we understood basics of resonance mechanisms. We observed RLC circuit response. We learnt how we can measure and calculate oscillation frequency f_d , and the decay time constant τ . We learnt how we find resistance for critically damped response.

Izmir Institute of Technology


Faculty of Engineering

HONOR CODE for EXAMS/HOMEWORKS

I am a student in the Department of f Electronics and Communcation Engineering with student ID number 250206039 I did not get help from anyone in answering these exam/homework questions and solving problems. I did not help anyone during the exam and did not share the results with anyone. While answering the questions, I followed ethical rules of conduct. I did not find solutions from the internet, copy someone else's information, or get help from any second party (academician, professional) or from an online source. In case the Lecturer declares that the exam or assignment is open book, open source, or open lecture notes, students still may not share information, work together or copy solutions from each other. What I write on the exam/homework paper is entirely my own knowledge. I know that if I am found to be in violation of these rules, an investigation will be launched against me according to the IZTECH discipline regulations.

Each student must send this Honor Code to his or her course instructor when submitting an exam or assignment. I agree that if I do not send this signed form to the instructor by e-mail with an exam or assignment, the instructor reserves the right **to not grade** the submitted paper.

Date:19/01/2021

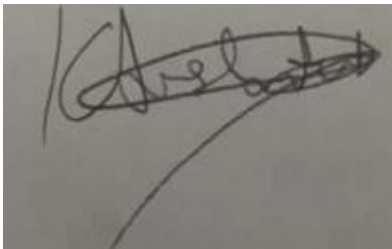A handwritten signature in dark ink, appearing to be 'Arslan', written over a light gray background.