

## EE203 - Electrical Circuits Laboratory

Experiment - 6 Simulation  
Operational Amplifiers

Name: Korkut Emre Arslantürk

Number: 250206039

Submission Date: 22/12/2020

## Preliminary Work

1. Refer to the LM741 datasheet and write the specified values for the following parameters.

Supply voltage range:  $\pm 18$  V


Input offset voltage: 2 V

Maximum power dissipation: 500mW

Input bias current: 80nA

Input voltage range:  $\pm 12$  VInput resistance: 20M $\Omega$ Output voltage range:  $\pm 14$  VOutput resistance: 75 $\Omega$ 

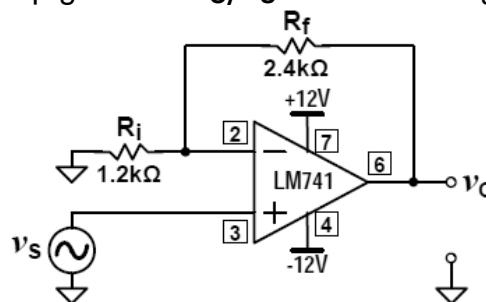2. Calculate the closed loop gain  $G = v_O/v_S$  of the following circuit.




This is summing amplifier so we can calculate with this formula :

$$V_s \left( 1 + \frac{R_f}{R_i} \right) = V_o \rightarrow G = \frac{V_o}{V_s} = 1 + \frac{R_f}{R_i}$$

$$R_f = 2.4k\Omega \quad R_i = 1.2k\Omega \quad \text{so} \quad G = \frac{V_o}{V_s} = 1 + \frac{2.4}{1.2} = 3$$

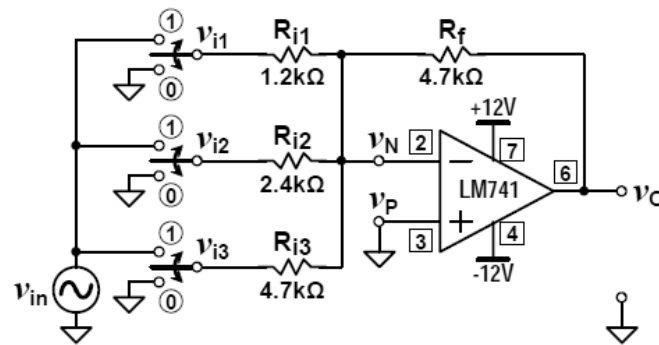3. Calculate the closed loop gain of the following summing amplifier for each of the three inputs,  $v_{i1}$ ,  $v_{i2}$ , and  $v_{i3}$ . Write an expression for  $v_o$  as a function of all inputs, and calculate the  $v_o$  amplitude for all switch positions listed in the table given for **step-2** of the procedure.



$$V_o = -R_f \left( \frac{V_{i1}}{R_{i1}} + \frac{V_{i2}}{R_{i2}} + \frac{V_{i3}}{R_{i3}} \right)$$

$$R_{i1} = 1.2k\Omega$$

$$R_{i2} = 2.4k\Omega$$

$$R_{i3} = 4.7k\Omega$$

$$R_f = 4.7k\Omega$$


$$\text{So, } V_o = -4.7k \left( \frac{V_{i1}}{1.2k} + \frac{V_{i2}}{2.4k} + \frac{V_{i3}}{4.7k} \right)$$

$V_{i1}$	$V_{i2}$	$V_{i3}$	$V_o$	$V_o$
0	0	0	0V	0V
0	0	1	-1V	1V
0	1	0	-1.96V	1.96V
0	1	1	-2.96V	2.96V
1	0	0	-3.92V	3.92V
1	0	1	-4.92V	4.92V
1	1	0	-5.86V	5.86V
1	1	1	-6.86V	6.86V

"-" → minus sign show us direction

4. An opamp circuit is required to generate the output,  $v_o = 3V + 3V \sin(\omega t)$ , when the input signal is  $v_{in} = 2V \sin(\omega t)$ . In other words, the input is amplified by 1.5x gain and a 3 V offset is added at the output.

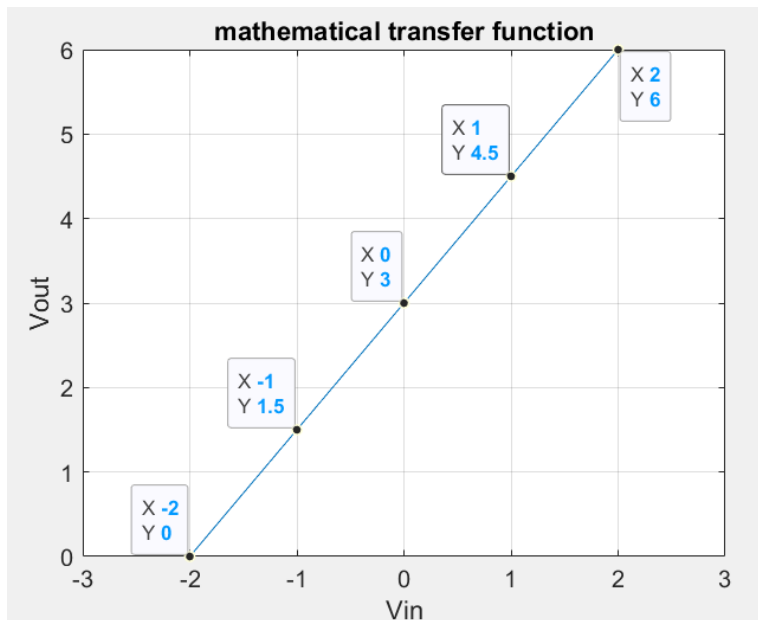a) Draw the mathematical transfer function, where horizontal axis shows the input for  $-3V < v_{in} < +3V$ , and vertical axis shows the corresponding output  $v_o$ .



b) Design this amplifier by using a single opamp,  $+12V$  and  $-12V$  supplies and resistors. All resistors must be  $>1k\Omega$  to prevent over-heating of the components. You should find solutions to the following questions.

Do you need an inverting or non-inverting amplifier?


How can you add the required offset by using  $+12V$  or  $-12V$  supply?

What should be the closed loop gain of the amplifier?

-We use non-inverting amplifier to get desired gain.

-We can add required offset through relationship between  $\pm 12V$  supplies and resistor values.

-It should be equal to 1.5.

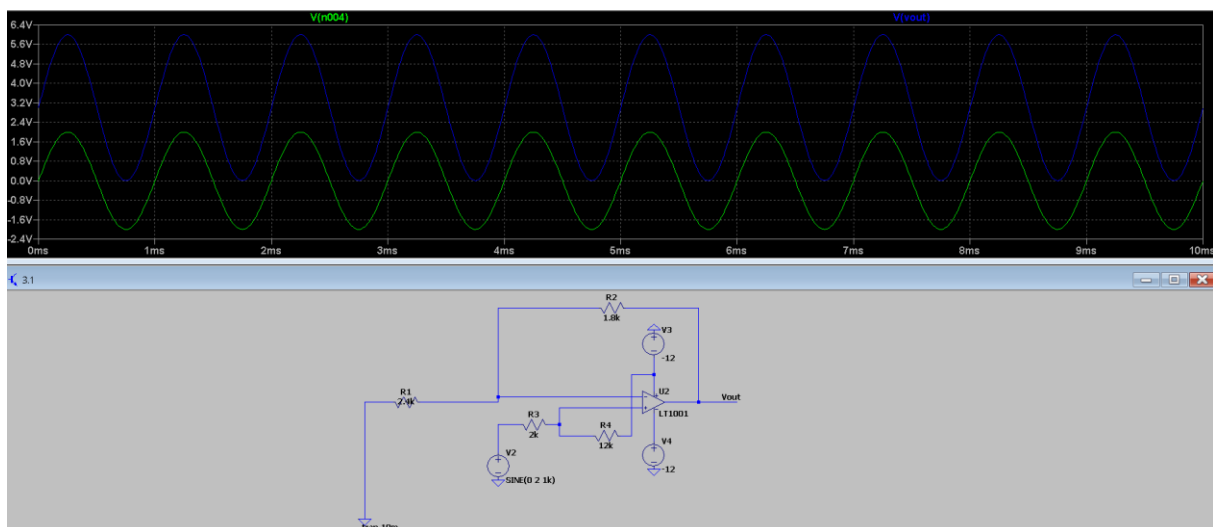

## Procedure

The model of **LT1001** operational amplifier will be used instead of **LM741** to obtain the simulation results on LTspice. Although **LT1001** has much better characteristics compared to **LM741**, both of the devices satisfy the basic requirements of an operational amplifier and the results obtained in the following steps will not be significantly different.

You should follow the instructions given below while working in laboratory and keep them in mind all the time even though there is no risk of damaging a component in simulation.

### Important Note:


**LM741** operational amplifier can be damaged easily if any of the specifications given in the **Absolute Maximum Ratings** section of the datasheet is exceeded. You must carefully follow the instructions given below in all parts of the experiment to minimize the risk of damaging the operational amplifier.

- ✓ Adjust DC supply and signal generator outputs without connecting them to the breadboard.
- ✓ Turned off DC supply and signal generator outputs before connecting them to your circuit.
- ✓ Check all circuit connections before turning on any of the sources. DC supply connections are the most critical.
- ✓ First turn on DC supplies, and then turn on signal generator.

Always turn off all sources before making changes in the circuit:

- ✓ First turn off signal generator, and then turn off DC supplies.
- ✓ Make the necessary changes in the circuit.
- ✓ First turn on DC supplies, and then turn on signal generator.

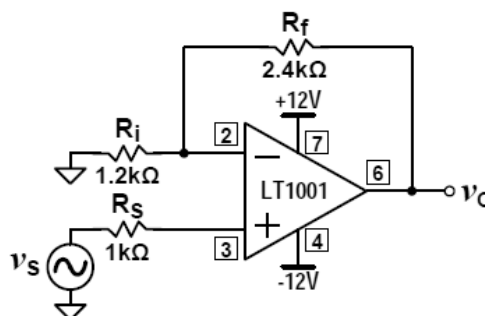1. Build the circuit given below. Place separate DC voltage sources to obtain **+12 V** and **-12 V** supplies required for the opamp. It is practical to connect these sources to net labels for each supply and use the same net labels for the opamp supply connections. Set the  $v_s$  signal source to obtain **1 kHz** sine wave with **1 V<sub>p-p</sub>** amplitude.



**1.1** Adjust  $v_S$  signal source to obtain the amplitudes in the following table and measure the corresponding  $v_O$  amplitudes on the oscilloscope.

$v_S$ amplitude (Vp-p)	$v_O$ amplitude (Vp-p)	voltage gain $ v_O / v_S $
1.0	2.99V	2.995
2.0	5.99V	2.995
3.0	8.985V	2.993
4.0	11.98V	2.995

We see linear relationship between  $v_S$  amplitude and  $v_O$  amplitude so that voltage gain is constant.

**1.2** Calculate the voltage gain for each  $v_S$  setting and record the result in the last column. Compare the results with the gain calculated in the preliminary work.

$v_S$ amplitude (Vp-p)	voltage gain $ v_O / v_S $	Calculated voltage gain in preliminary work	%Error
1.0	2.995	3	0.16
2.0	2.995	3	0.16
3.0	2.993	3	0.23
4.0	2.995	3	0.16


We can see our percentage of error is fewer than 1 for each  $V_S$  amplitude. Our little bit error can be cause of decimal rounding.

**1.3** Gradually increase the  $v_S$  amplitude until you see clipping distortion in the  $v_O$  waveform. Record the  $v_S$  and  $v_O$  amplitudes at the onset of distortion.

$$|v_S| = 7.4 \text{ V}_{p-p}$$

$$|v_O| = 21.92 \text{ V}_{p-p}$$

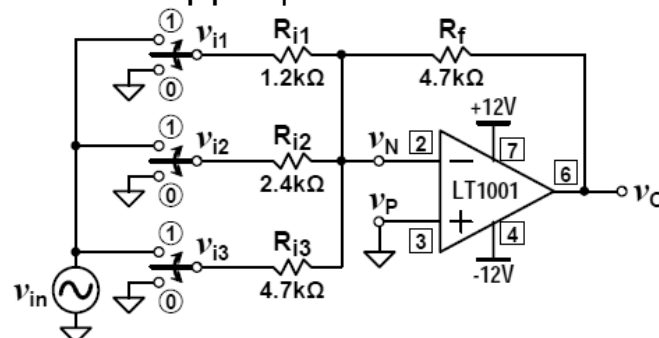**2.** Build the following summing amplifier circuit and adjust the  $v_{in}$  signal source to obtain **1 kHz** sine wave with **1 Vp-p** amplitude.



**2.1** This circuit is a simple **digital-to-analog converter** that generates an output proportional to the binary number given by the **0** or **1** switch positions. Measure and record the output voltage  $v_o$  for the sequence of input voltage combinations shown in the following table. Connect the input resistors,  $R_{i1}$ ,  $R_{i2}$ , and  $R_{i3}$  either to ground or to the signal source output to obtain the input amplitudes listed in the table.

switch positions	input amplitudes ( $V_{p-p}$ )			measured $v_o$ amplitude ( $V_{p-p}$ )	calculated $v_o$ amplitude ( $V_{p-p}$ )	%Error
	$v_{i1}$	$v_{i2}$	$v_{i3}$			
<b>0 0 0</b>	0	0	0	0	0	0
<b>0 0 1</b>	0	0	1	997.18359mV	1V	0.28
<b>0 1 0</b>	0	1	0	1.95V	1.96V	0.51
<b>0 1 1</b>	0	1	1	2.95V	2.96V	0.34
<b>1 0 0</b>	1	0	0	3.91V	3.92V	0.26
<b>1 0 1</b>	1	0	1	4.91V	4.92V	0.20
<b>1 1 0</b>	1	1	0	5.85V	5.86V	0.17
<b>1 1 1</b>	1	1	1	6.85V	6.86V	0.15

**2.2** Compare the measured values with the output amplitudes calculated in the preliminary work.

In previous table we can see our percentage of error fewer than 1 between measured values and calculated values in preliminary work. Our little bit error can be due to decimal rounding.


**3.** Build the circuit you designed for question **4** of the preliminary work.

**3.1** Measure the output voltage for the input voltage settings given in the following table to verify how well your design is working. You need to figure out a way to create **+2 V** and **-2 V DC** for your inputs.

DC voltage (V) at $v_{in}$	measured $v_o$ (V)	expected $v_o$ (V)	%error
-2.0	0V	0	0.0
-1.0	1.49V	1.5	0.66
0.0	2.99V	3	0.33
+1.0	4.53V	4.5	0.66
+2.0	5.99V	6	0.16

According to table we can see our percentage of error fewer than 1 between measured values and expected values. Our little bit error may be due to cursor putting error while measuring.

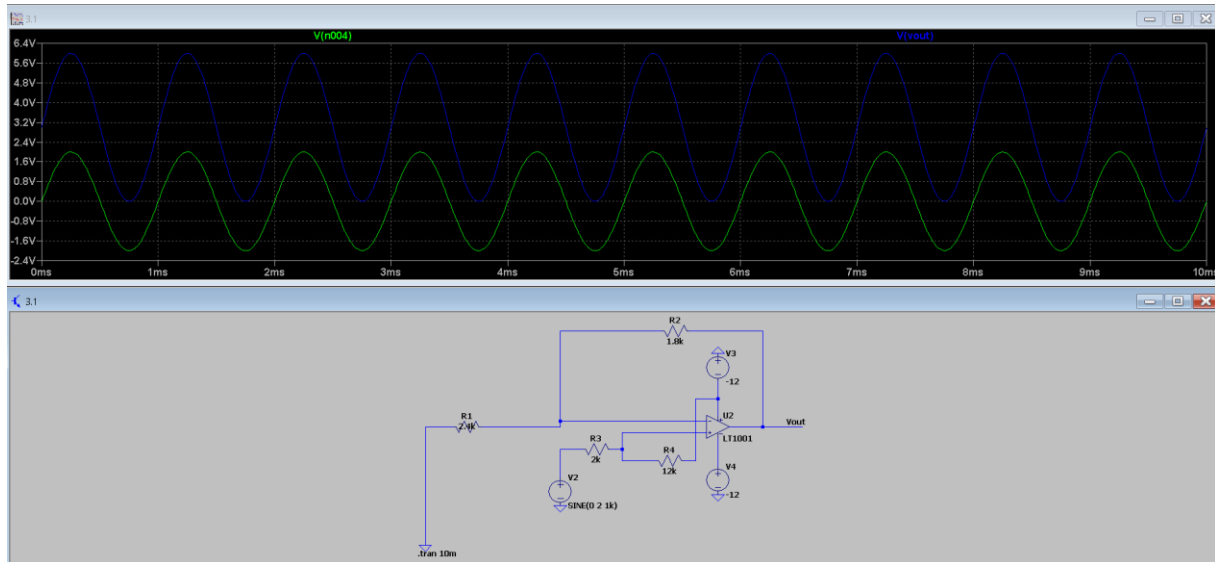**3.2** Use the signal generator to obtain a **1 kHz 4 V<sub>p-p</sub>** (**-2 V to +2 V**) sine wave input signal and observe the output of your circuit. Comment on the results.



Our  $V_{in}(V_{p-p})=3.99$  and  $V_{out}(V_{p-p})=5.98V$  so our gain is almost equal to 1.5 so we can say it does not depends on frequency. We can say our  $V_{out}$  is between 0-6V and we can say  $V_O = 3V + 3V \sin(\omega t)$ , Our output voltage value is almost same for different input values as previous step(3.1).

## Conclusion

In this experiment, in preliminary work, firstly we examined LM741 datasheet, then we calculated closed loop gain for given circuit. After that we calculated the closed loop gain of the given summing amplifier for each of the three inputs, and we calculated the  $V_O$  amplitude for all switch positions. Then we designed a circuit according the desired  $V_{in}$  and  $V_{out}$  values. We draw the mathematical transfer function  $V_{in}$  and  $V_{out}$ . In first part, we built given circuit and we measured  $V_O(V_{p-p})$  amplitude and we calculate voltage gain for different  $V_s$  amplitudes(1V,2V,3V,4V) and when we compare measured voltage gain with calculated voltage gain in preliminary work we see we get almost same result. After that, we increase  $V_s$  amplitude until to see distortion. In second part, we built given digital to analog converter circuit and we adjust 1kHz sine wave with 1V<sub>p-p</sub> amplitude. We measured  $V_O$  amplitude for each switch position and we compared them with our calculated values is preliminary work and we see we get almost same results. Then we set a circuit which we design in preliminary work and we measured  $V_O$  for different DC voltage at  $V_{in}$ (-2V to 2V).

To sum up in this experiment, we applied analysis methods for closed loop circuits. We observed closed loop response of operational amplifiers. We see limitations of operational amplifiers.

## Questions

**Q1.a)** What would happen to  $v_o$ , if  $R_S = 1 \text{ k}\Omega$  is replaced by a  $100 \Omega$  resistor or a  $10 \text{ k}\Omega$  resistor in the circuit built for step 1? Why?

If we replaced by a  $100 \Omega$  resistor or a  $10 \text{ k}\Omega$  resistor in the circuit built for step 1, we would not see any change for  $v_o$ . Ideal op-amp has infinite resistance between node p and n, so that the input current into the node p is equal to zero, because of that we have zero voltage on the resistor so  $R_S$  value does not affect  $V_o$ .

**b)** What is the usage of  $R_S = 1 \text{ k}\Omega$  in step-1 of this experiment?

The usage of this resistor show us that ideal op-amp has infinite resistance between node p and n so there is no current on  $R_S$  and so  $R_S$  does not affect  $V_o$ .

**Q2.** You observed a clipping distortion at the output in step 1.3. Which specification in the **LM741** datasheet can help you predict the voltage level at the onset of clipping distortion? How?

According to datasheet when supply voltages are  $\pm 15\text{V}$ , the peak-to-peak output voltage swing shows that the op-amp usually saturates at least  $\pm 10 \text{ V}$  and also  $\pm 13 \text{ V}$ , if the load resistor is greater than  $2 \text{ k}\Omega$ . The output voltage of '22 V' with a  $\pm 12 \text{ V}$  DC supply was observed. In part 1.3 we found distortion for  $21.92\text{V}$  so our percentage of error is just 0.3.

**Q3.** What are the advantages of using operational amplifiers in circuit design?  
We use operational amplifiers in circuit design

There are many advantages to using an operational amplifier. We use operational amplifiers in circuit design to increase gain. Op-amps can be used in many different areas and goals like as universal amplifiers, precision rectifiers, analogue to digital and digital to analogue converters, filters, differentiators and integrators, voltage and current regulators.



**Izmir Institute of Technology****Faculty of Engineering****HONOR CODE for EXAMS/HOMEWORKS**

I am a student in the Department of Electronics and Communication Engineering with student ID number 250206039. I did not get help from anyone in answering these exam/homework questions and solving problems. I did not help anyone during the exam and did not share the results with anyone. While answering the questions, I followed ethical rules of conduct. I did not find solutions from the internet, copy someone else's information, or get help from any second party (academician, professional) or from an online source. In case the Lecturer declares that the exam or assignment is open book, open source, or open lecture notes, students still may not share information, work together or copy solutions from each other. What I write on the exam/homework paper is entirely my own knowledge. I know that if I am found to be in violation of these rules, an investigation will be launched against me according to the IZTECH discipline regulations.

Each student must send this Honor Code to his or her course instructor when submitting an exam or assignment. I agree that if I do not send this signed form to the instructor by e-mail with an exam or assignment, the instructor reserves the right **to not grade** the submitted paper.

Date:29/12/2020

Signature:

A photograph of a handwritten signature in black ink on a light-colored surface. The signature is stylized and appears to be 'B. Özdemirel'.