

## EE203 – Electrical Circuits Laboratory Experiment 2 Laboratory Report Time-Varying Signals

### Group Members:

Name: Korkut Emre Arslantürk

Number: 250206039

Submission Date: 17/11/2020


## Preliminary Work

1. Read the procedure given for this experiment, and make sure that you have the required knowledge about the laboratory equipment to perform the specified steps in case you need to make the measurements with real components and devices. Refer to EELab\_GuideBeginner.pdf to refresh your memory. Read the section titled Grounding of Test Equipment, regarding monitoring of differential voltages with an oscilloscope.


2 Open a new schematic file in LTspice and place a voltage source with a net label at its positive output as shown below.

Set the Vsrc parameters to obtain the following waveforms. Verify the voltage output by displaying the voltage at the src node after running a simulation.

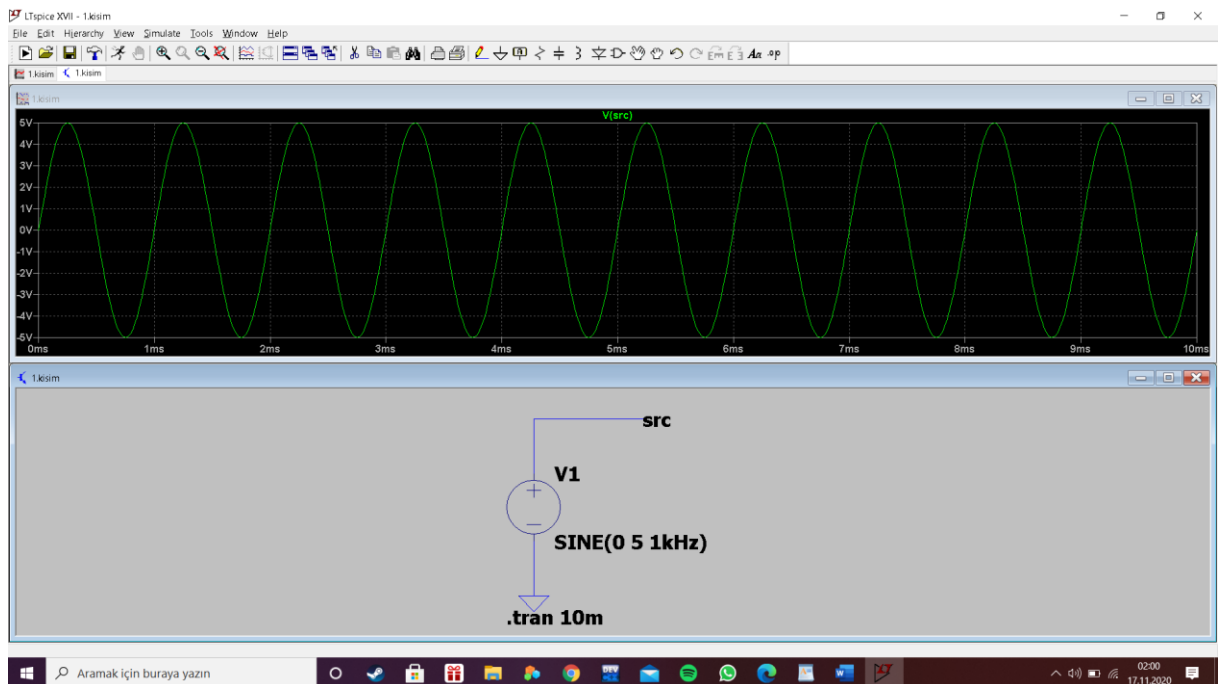
a) 1 kHz sinusoidal signal with 10 Vp-p amplitude and 0 V DC offset



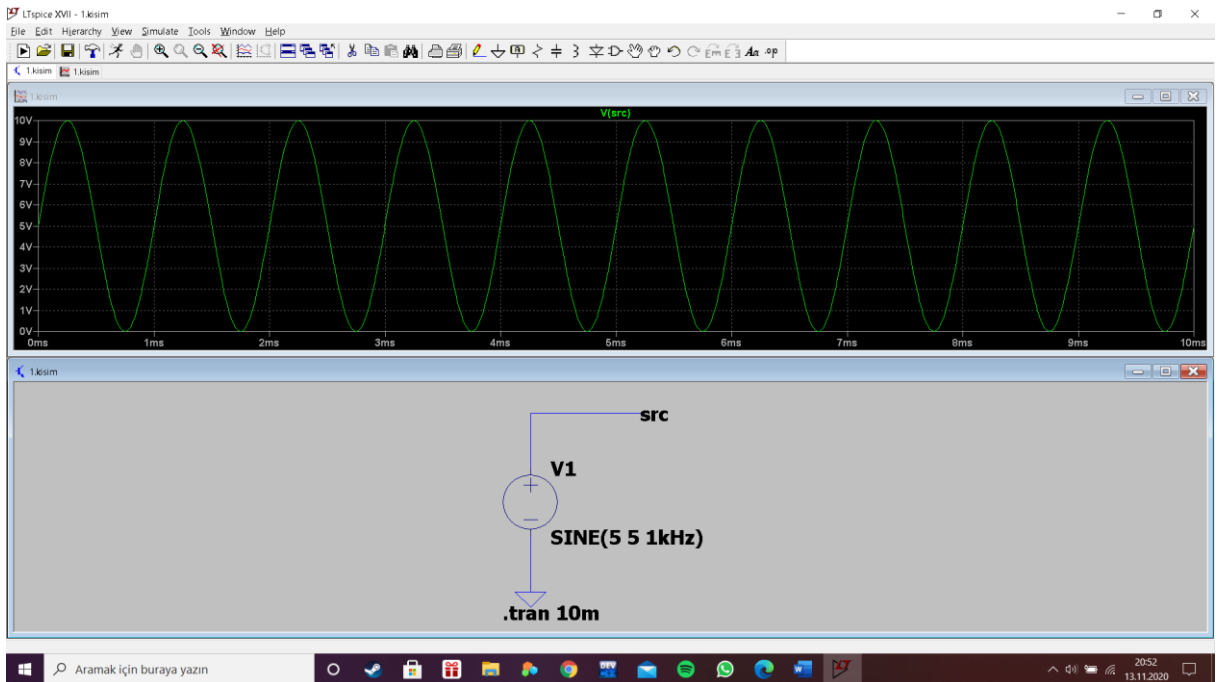
b) 1 kHz sinusoidal signal with 10 Vp-p amplitude and 5 V DC offset



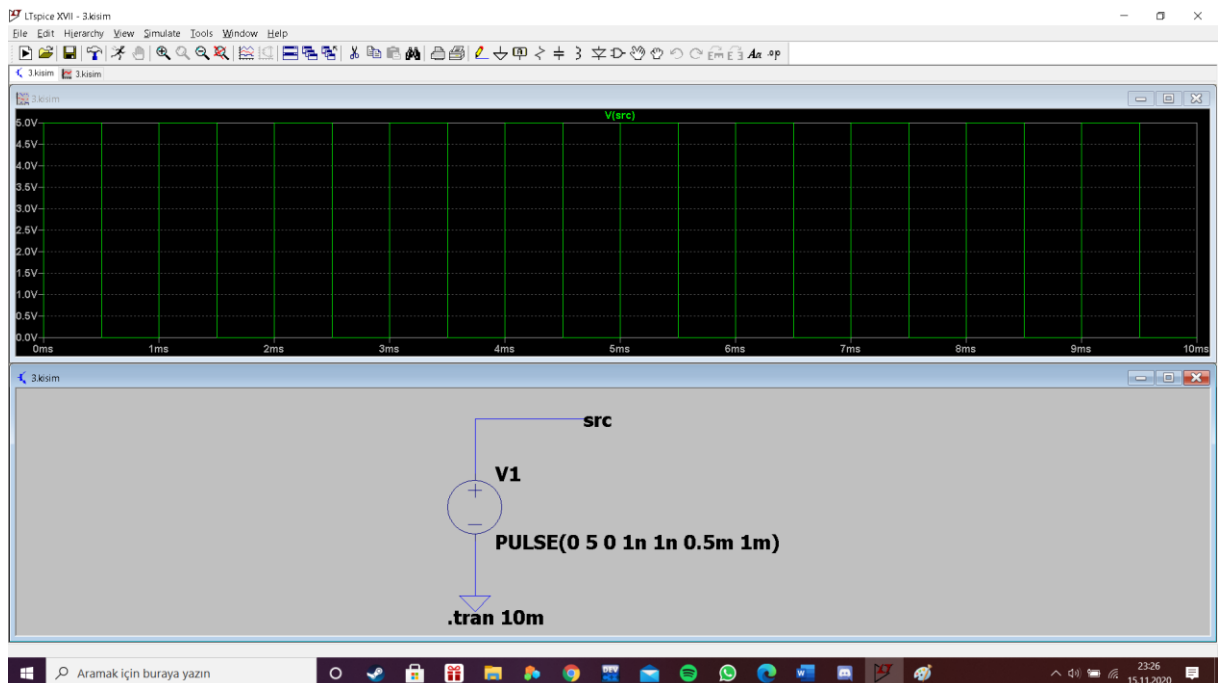
c) 1 kHz pulse waveform that changes between 0 V and 5 V with 50% duty cycle



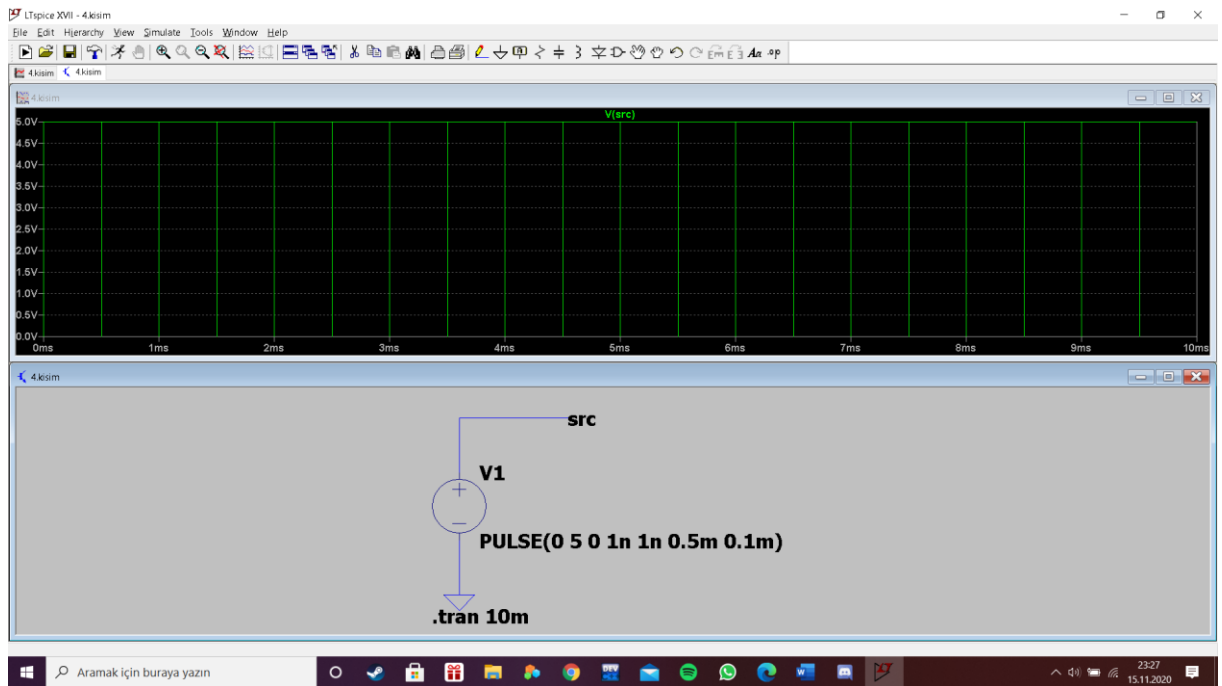- d) 10 kHz pulse waveform that changes between 0 V and 5 V with 50% duty cycle




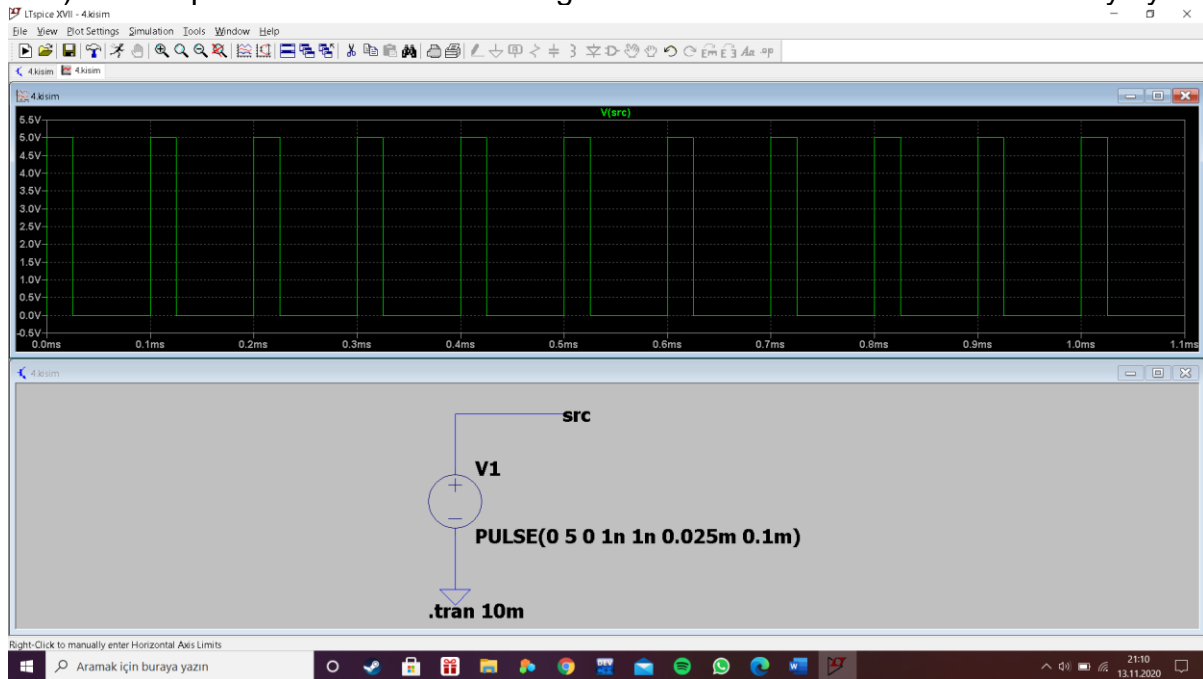- e) 10 kHz pulse waveform that changes between 0 V and 5 V with 25% duty cycle



## Results

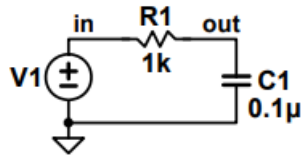- 1.1** Build the circuit shown below on LTspice. Enter the C1 capacitor value as 0.1u (with the letter "u") or 100n. The C1 capacitor is necessary just to obtain different waveforms from a single voltage source. You will not make any calculations with C1




- 1.2** Set the V1 signal to **5 V sin(2π 1000 t)**. Right-click on the V1 voltage source, click on the **Advanced** button and select the **SINE** option to obtain a **1 kHz** sinusoidal signal with 0 V offset and 5 V peak amplitude. The component value of V1 should appear as **"SINE(0 5 1k)"** on the schematic. Place the net labels **"in"** and **"out"** as shown in the figure.

- 1.3** Enter the SPICE directive **".tran 10m"** to set the simulation time to **10 ms**. Run the simulation with the V1 frequency and R1 settings listed in the following table. Measure the peak-to-peak amplitude of **V<sub>out</sub>** and its time delay relative to **V<sub>in</sub>**, and calculate **V<sub>out</sub>** phase.

| V1 Frequency (kHz) | R1(kΩ) | V <sub>out</sub> amplitude (V <sub>p-p</sub> ) | V <sub>out</sub> delay(ms) | V <sub>out</sub> phase (degree) |
|--------------------|--------|--|----------------------------|---------------------------------|
| 1.0                | 1.0    | 8.44V  | 0.092ms                    | 33.12                           |
| 1.0                | 3.3    | 4.33V  | 0.184ms                    | 66.24                           |
| 1.0                | 10.0   | 1.57V  | 0.231ms                    | 83.16                           |
| 3.3                | 1.0    | 3.95V  | 0.055ms                    | 65.35                           |
| 3.3                | 3.3    | 1.42V  | 0.068ms                    | 80.79                           |
| 3.3                | 10.0   | 0.47V  | 0.075ms                    | 89.11                           |
| 10.0               | 1.0    | 1.44V  | 0.023ms                    | 82.8                            |
| 10.0               | 3.3    | 0.44V  | 0.0241ms                   | 86.76                           |
| 10.0               | 10.0   | 0.15V  | 0.0257ms                   | 92.52                           |

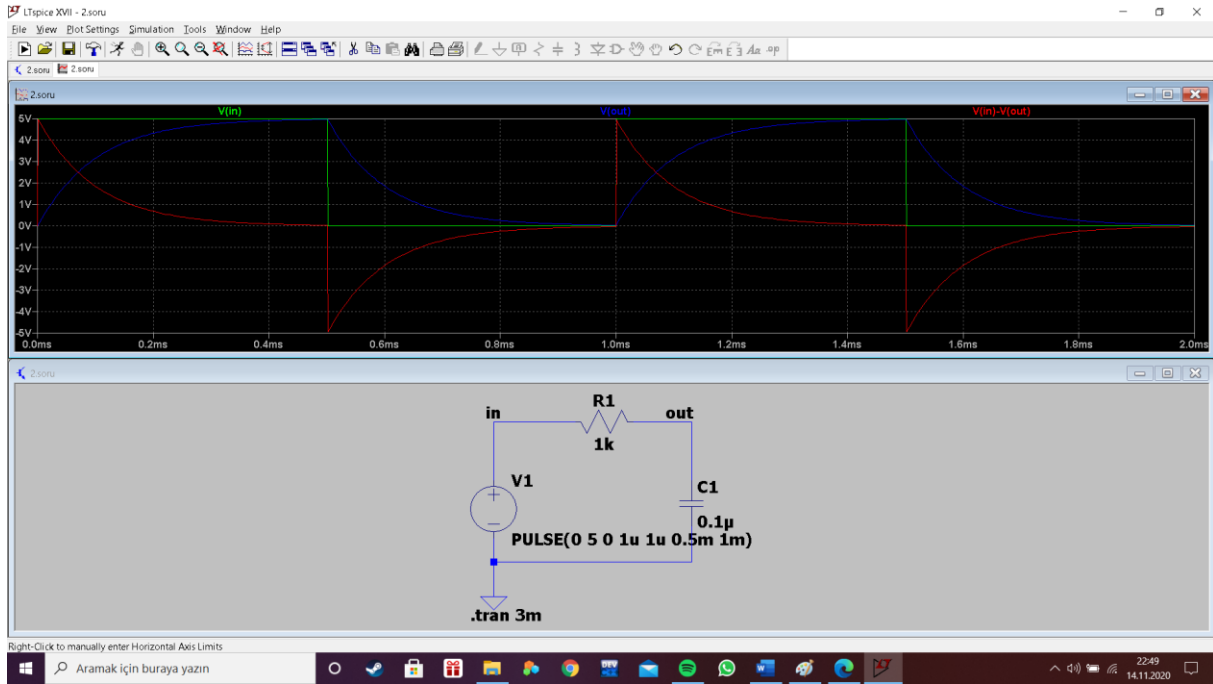
2.1 Change the **V1** source to obtain a **1 kHz** pulse waveform. Right-click on the **V1** voltage source, select the **PULSE** option, and enter the following parameters:  $V_{initial} = 0$ ,  $V_{on} = 5$ ,  $T_{delay} = 0$ ,  $T_{rise} = 1\mu$ ,  $T_{fall} = 1\mu$ ,  $T_{on} = 0.5m$ ,  $T_{period} = 1m$



2.2 Measure the three voltages displayed on the waveform window at the time instants specified in the following table.

| Time of measurement                | $V_{in}(V)$ | $V_{out}(V)$ | $V_{in}(V) - V_{out}(V)$ |
|------------------------------------|-------------|--------------|--------------------------|
| right after $V_{in}$ rising edge   | 5V          | 58mV         | 4.941V                   |
| middle of $V_{in}$ ON (5V) cycle   | 5V          | 4.59V        | 409mV                    |
| right before $V_{in}$ falling edge | 5V          | 4.96V        | 0.4V                     |
| right after $V_{in}$ falling edge  | 0V          | 4.94V        | -4.94V                   |
| middle of $V_{in}$ OFF (0V) cycle  | 0V          | 414.50mV     | -414.50mV                |
| right before $V_{in}$ rising edge  | 0V          | 33.96mV      | -33.96mV                 |

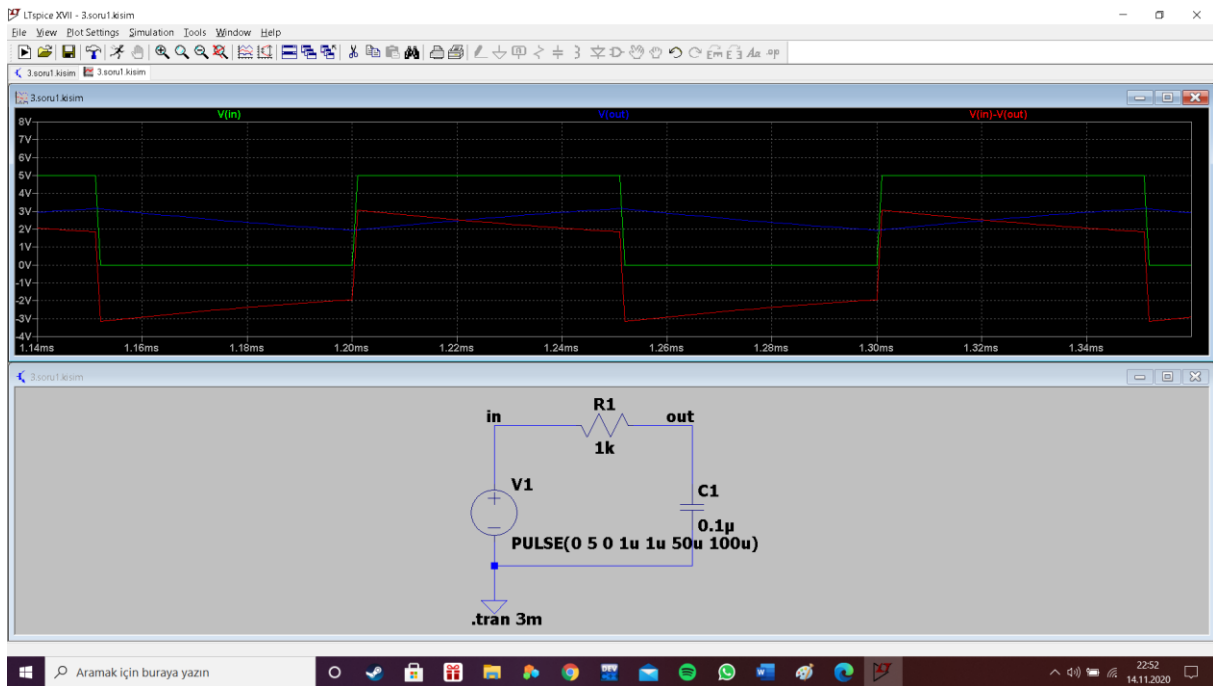
2.3 Repeat part 2.2 after changing pulse frequency to **10 kHz** (set the V1 source parameters:  $T_{on} = 50\mu$ ,  $T_{period} = 100\mu$ ).




Measure the three voltages displayed on the waveform window at the time instants specified in the following table.

| Time of measurement                | $V_{in}(V)$ | $V_{out}(V)$ | $V_{in}(V) - V_{out}(V)$ |
|------------------------------------|-------------|--------------|--------------------------|
| right after $V_{in}$ rising edge   | 5V          | 1.95V        | 3.05V                    |
| middle of $V_{in}$ ON (5V) cycle   | 5V          | 2.625V       | 2.375V                   |
| right before $V_{in}$ falling edge | 5V          | 3.15V        | 1.85V                    |
| right after $V_{in}$ falling edge  | 0V          | 3.144V       | -3.144V                  |
| middle of $V_{in}$ OFF (0V) cycle  | 0V          | 2.475V       | -2.475V                  |
| right before $V_{in}$ rising edge  | 0V          | 1.94V        | -1.94V                   |

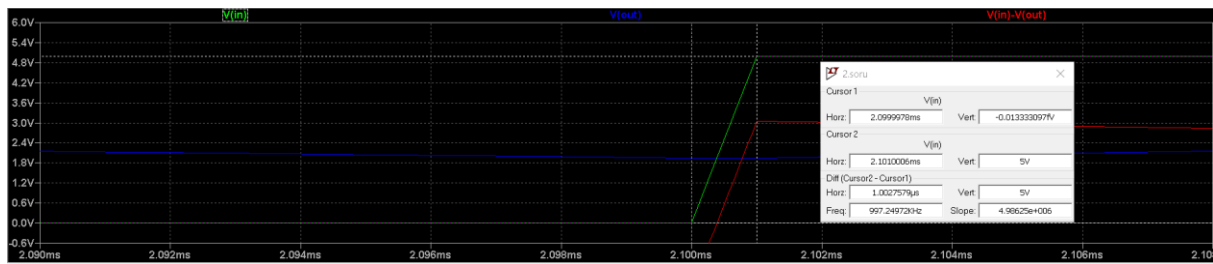3.1 Zoom into the rising edge of the  $V_{in}$  waveform repeatedly until you can clearly identify the linear ramp from  $0\text{ V}$  to  $5\text{ V}$ . Measure the rise time from  $0\text{ V}$  to  $5\text{ V}$  and verify the **Trise** setting of the voltage source. Similarly, zoom into the falling edge of the  $V_{in}$  waveform and measure the fall time.




$$T_{rise} = 1.002\mu s$$

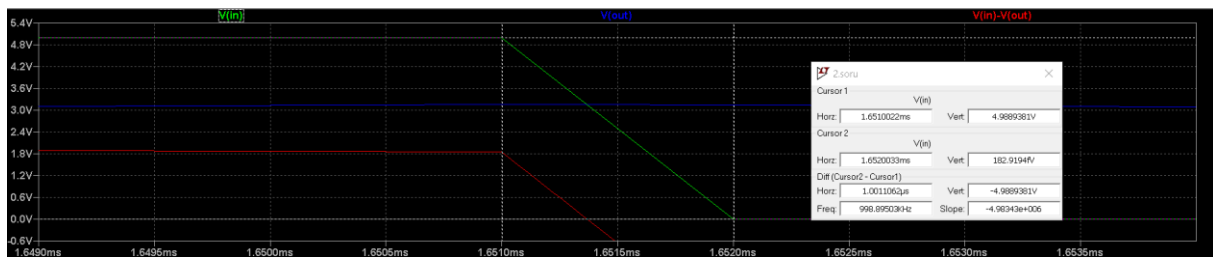


$$T_{fall} = 1.001\mu s$$

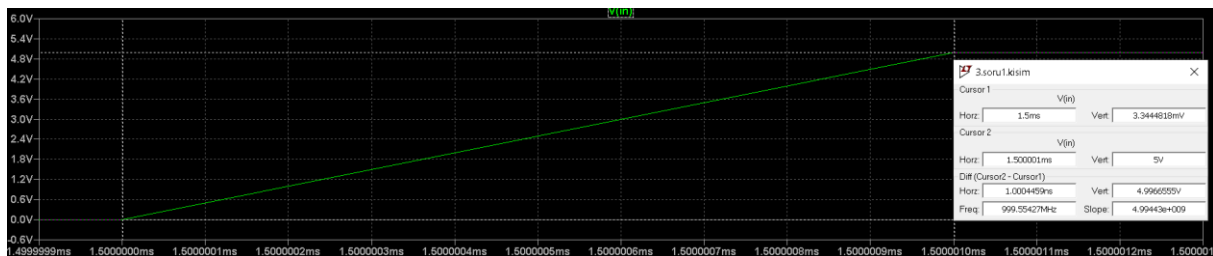3.2 Right-click on the value text "**PULSE(0 5 0 1u 1u 50u 100u)**" of V1 source on the schematic and enter a new value given by "**PULSE(0 5 0 1n 1n 50u 100u)**". Run simulation and repeat the rise time and fall time measurements on the vin waveform.



$$T_{rise} = 1.00ns$$

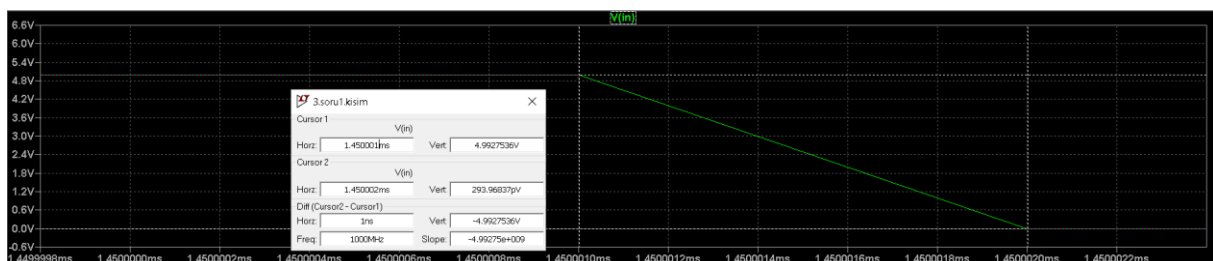

$$T_{fall} = 1.00ns$$

## Conclusion

In this experiment, In preliminary work, we place a voltage source and we set it first to get 1 kHz sinusoidal signal with 10 Vp-p amplitude and 0 V DC offset then we change 5V DC offset. Then we set as 1 kHz pulse waveform that changes between 0 V and 5 V with 50% duty cycle. After that we changed frequency 1kHz to 10kHz and finally we changed duty cycle to 25%. In first part, we built a circuit using voltage source, 1k $\Omega$  resistor and 0.1 $\mu$  capacitor. Then, we set the  $V_1$  signal to  $5V\sin(2\pi 1000t)$ . After that we calculated the  $V_{out}$  amplitude( $V_{p-p}$ ),  $V_{out}$  delay and  $V_{out}$  phase values by changing the frequency (1.0kHz-3.3kHz-10.0kHz) and resistance values(1k $\Omega$ -3.3 k $\Omega$ -10k $\Omega$ ), step by step. In second part, we built same circuit with before part but we change voltage source to obtain a 1 kHz pulse waveform. We entered following parameters  $V_{initial} = 0$ ,  $V_{on} = 5$ ,  $T_{delay} = 0$ ,  $T_{rise} = 1\mu$ ,  $T_{fall} = 1\mu$ ,  $T_{on} = 0.5m$ ,  $T_{period} = 1m$ . After that, we display  $V_{in}$ ,  $V_{out}$  and  $V_{in}-V_{out}$  and we measured  $V_{in}$ ,  $V_{out}$  and  $V_{in}-V_{out}$  on right after  $v_{in}$  rising edge, middle of  $v_{in}$  ON (5V) cycle, right before  $v_{in}$  falling edge, right after  $v_{in}$  falling edge, middle of  $v_{in}$  OFF (0V) cycle, right before  $v_{in}$  rising edge using cursor. In next step, we changed frequency 1kHz to 10kHz,  $T_{on} = 50\mu$ ,  $T_{period} = 100\mu$  and we repeated same display and measurement. In third part, first we measured the rise time from 0V to 5V and verified the  $T_{rise}$  setting of the voltage source and then we repeated same calculation for falling time. Then, we change to values from "PULSE(0 5 0 1u 1u 50u 100u)" to "PULSE(0 5 0 1n 1n 50u 100u)" and we repeated the rise time and fall time measurements on the  $V_{in}$  waveform.

To sum up in this experiment, we learnt parameters that describe time-varying signals, what is the peak amplitude( $V_{peak}$ ), peak-to-peak amplitude( $V_{p-p}$ ), period, delay time and phase. We learnt how we calculate them. Then we learnt pulse waveform parameters, what is the  $T_{on}$  and  $T_{off}$ , we learnt how we calculate duty cycle using them. We learnt what is the falling edge and rising edge and how we measure  $T_{rise}$  and  $T_{fall}$ . We become familiar with measurement of time-varying signal parameters.



# Answers

**Q1.** Describe the variations in  $v_{out}$  amplitude and phase as a function of  $R1$  when the  $v_{in}$  frequency is 10 kHz in step-2 of the experiment. Predict the  $v_{out}$  amplitude and phase that will be obtained at 10 kHz when  $R1$  is 100 k $\Omega$ .

We can get estimate value for this equation:

$$V_{out} = \frac{1.44}{R1}$$

And using this equation for  $R1$  is 100 k $\Omega$ ,  
our expected  $v_{out}$  amplitude( $V_{p-p}$ )= $1.44/100=0.0144V$




Our calculated  $v_{out}$  amplitude= $0.01463V$  and  
our expected  $v_{out}$  amplitude= $0.0144V$  so our percentage error is just 1.6.

About phase, we can see at frequency constant, when resistor increasing phase increasing but when resistor increasing rate increase, phase increasing rate decreasing(because of that we can say it will be logarithmic function according to resistance value). Thus, for  $R1$  is 100 k $\Omega$ , we can expect phase increasing but not so much so it will be bigger than 92.52 and when we calculate we see phase is 93.62 so our expectation is true.

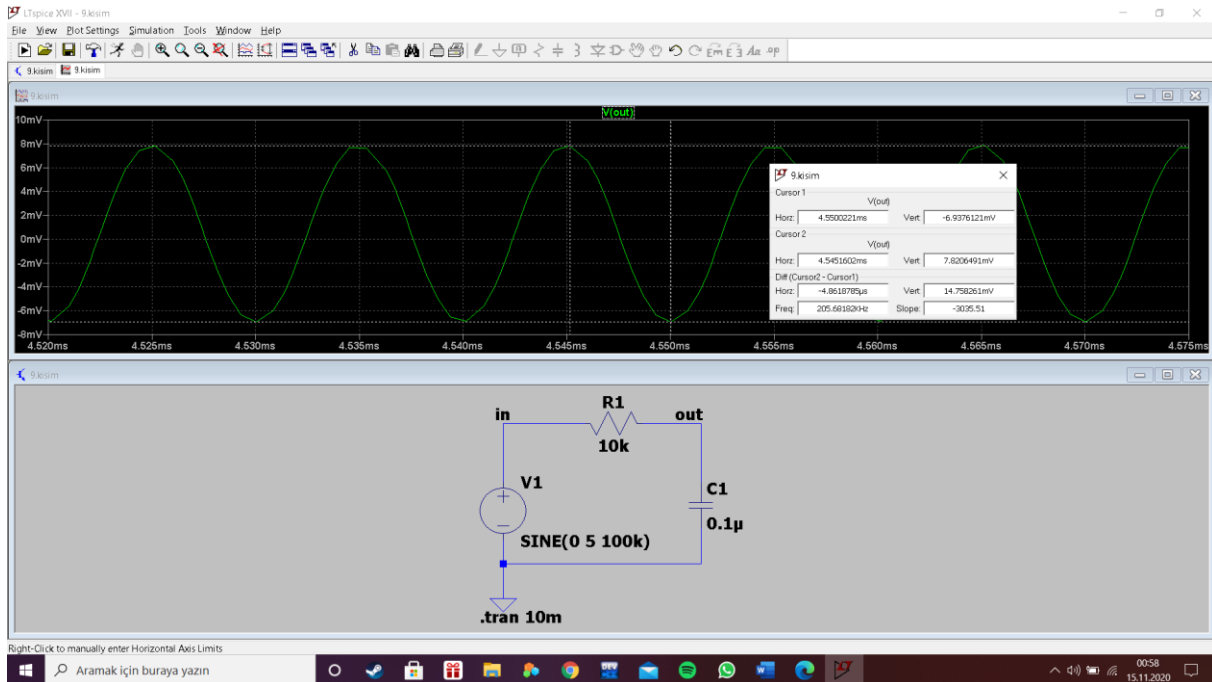**Q2.** Describe the variations in  $v_{out}$  amplitude and phase as a function of  $v_{in}$  frequency when  $R_1$  is 10 k $\Omega$  in step-2 of the experiment. Predict the  $v_{out}$  amplitude and phase that will be obtained at 100 kHz when  $R_1$  is 10 k $\Omega$ .

We can say,  $V_{out}$  amplitude( $V_{p-p}$ )= 1.57/ $V_{in}$  frequency so our expected  $V_{out}$  at 100 kHz is 0.0157V.



Our calculated  $v_{out}$  amplitude=0.0146V and our expected  $v_{out}$  amplitude=0.015V so our percentage error is just 2.6.



About phase, we can see at resistance constant, when frequency increasing phase increasing but when frequency increasing rate increase, phase increasing rate decreasing(because of that we can say it will be logarithmic function according to frequency value). Thus, for frequency is 100 kHz, we can expect phase increasing but not so much so it will be bigger than 92.52 and when we calculate we see phase is 93.64 so our expectation is true.

**Q3.** Compare the  $V_{out}$  amplitude and phase obtained in step-2 of the experiment for the couple of settings given below.

**setting 1:**  $V_{in}$  frequency = 1 kHz,  $R1 = 10\text{ k}\Omega$

**setting 2:**  $V_{in}$  frequency = 10 kHz,  $R1 = 1\text{ k}\Omega$

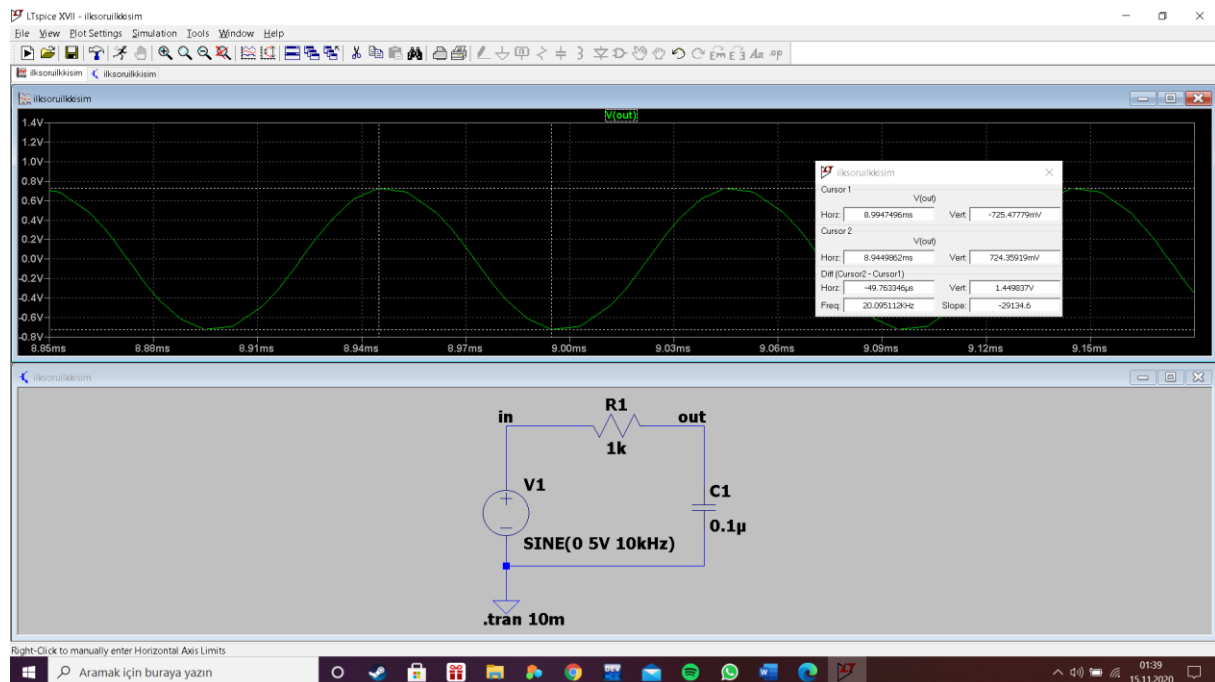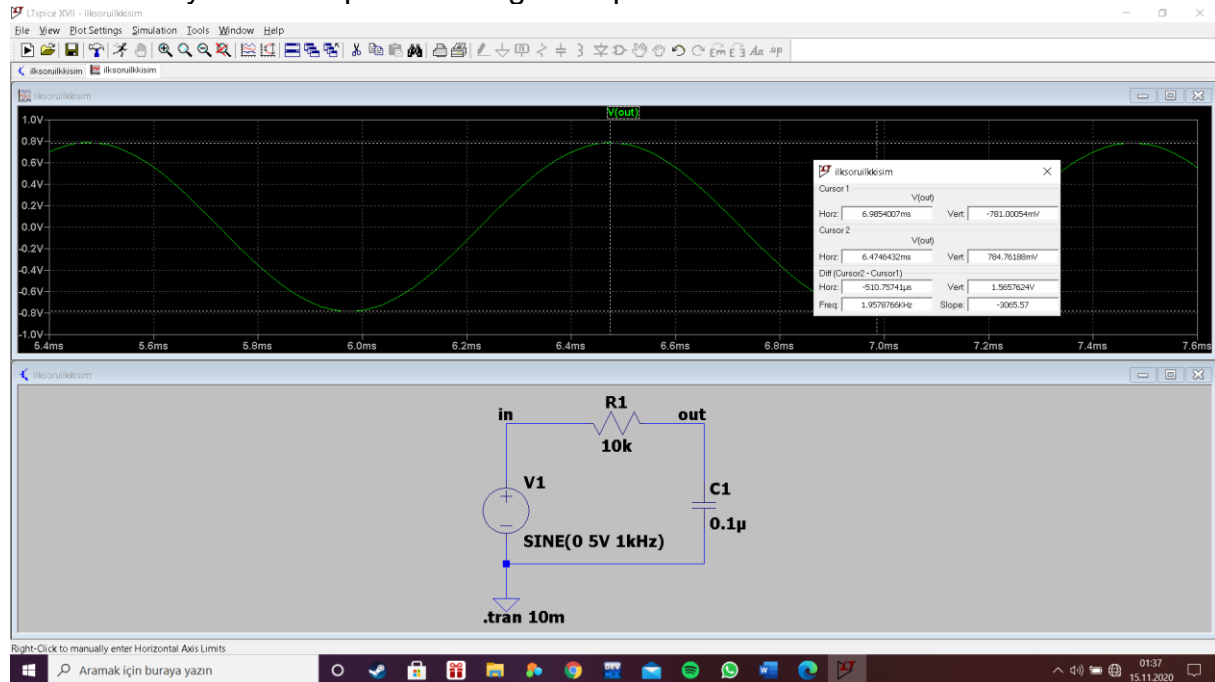Are there any other couple of settings that produced similar results?



For example if we use  $V_{in}$  frequency = 100 Hz,  $R1 = 100\text{ k}\Omega$ , our  $V_{out}$  amplitude( $V_{p-p}$ ) will be 1.75V or  $V_{in}$  frequency = 100k Hz,  $R1 = 100\Omega$ , our  $V_{out}$  amplitude( $V_{p-p}$ ) will be 1.44V. We can see when we multiply a constant one of them, if we divided by other of them with same constant we will calculate close results.

**Q4.** Verify that the voltage measurements recorded in step 2.2 and 2.3 are in accordance with the Kirchhoff's Voltage Law. Explain any discrepancies.

| Time of measurement                | $V_{in}(V)$ | $V_{out}(V)$ | $V_{in}(V) - V_{out}(V)$ |
|------------------------------------|-------------|--------------|--------------------------|
| right after $V_{in}$ rising edge   | 5V          | 58mV         | 4.941V                   |
| middle of $V_{in}$ ON (5V) cycle   | 5V          | 4.59V        | 409mV                    |
| right before $V_{in}$ falling edge | 5V          | 4.96V        | 0.4V                     |
| right after $V_{in}$ falling edge  | 0V          | 4.94V        | -4.94V                   |
| middle of $V_{in}$ OFF (0V) cycle  | 0V          | 414.50mV     | -414.50mV                |
| right before $V_{in}$ rising edge  | 0V          | 33.96mV      | -33.96mV                 |

Table 2.2

| Time of measurement                | $V_{in}(V)$ | $V_{out}(V)$ | $V_{in}(V) - V_{out}(V)$ |
|------------------------------------|-------------|--------------|--------------------------|
| right after $V_{in}$ rising edge   | 5V          | 1.95V        | 3.05V                    |
| middle of $V_{in}$ ON (5V) cycle   | 5V          | 2.625V       | 2.375V                   |
| right before $V_{in}$ falling edge | 5V          | 3.15V        | 1.85V                    |
| right after $V_{in}$ falling edge  | 0V          | 3.144V       | -3.144V                  |
| middle of $V_{in}$ OFF (0V) cycle  | 0V          | 2.475V       | -2.475V                  |
| right before $V_{in}$ rising edge  | 0V          | 1.94V        | -1.94V                   |

Table 2.3

Kirchhoff's Voltage Law states that for a closed loop series path the algebraic sum of all the voltages around any closed loop in a circuit is equal to zero. When we look at the circuit, we saw 3 voltage:  $V_{in}$ ,  $V_{out}$ ,  $V_r$ .  $V_r$  is equal to  $V_{in} - V_{out}$  and because of ..To verify rule, this equation must be true  $V_{in} = V_{in} - V_{out} + V_{out}$  and when we look at the table we can see this condition is true, some of rows we can see %0.01 error this is about decimal rounding while doing calculation.

**Q5.** In a practical laboratory environment,  $V_1$  voltage source will be a signal generator. What happens if you try to monitor the voltage across  $R_1$  by using a single oscilloscope probe as shown below? Why?

If we do that, we will measure Voltage on resistor on the other words, we will measure  $V_{in} - V_{out}$ . When we measure normally, we touch voltage source with one part of probe and we touch ground with other part of probe and we know ground is 0V but in this situation it will have voltage value.